



Srini Science Mind
Abdul Kalam Physical Science Group



NEW

10th class

PHYSICAL SCIENCE


MODEL LESSON PLAN



M.SRINIVASA RAO, SA(PS) AGKMHS GUDIVADA PH: 9848143855

TEACHING LEARNING PROCESS

Induction/Introduction:

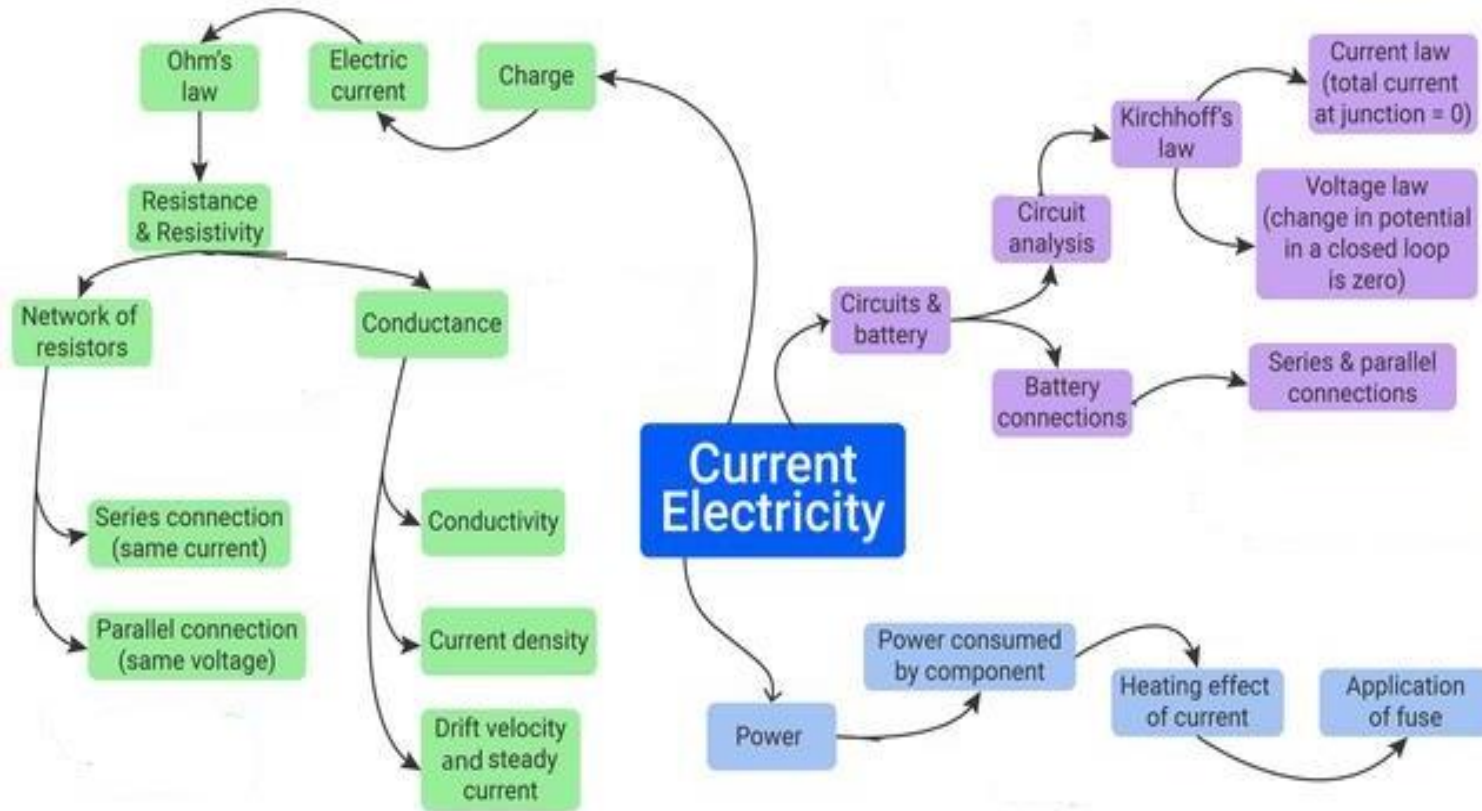

Experience and Reflection:

1. Students will learn why Kirchhoff's laws apply to DC circuits.
2. Students will combine and use electrical devices in the best manner according to their needs in daily life.
3. Students will learn what precautions to take in case of electric shock when connecting electrical equipment.

Explicit Teaching/Teacher Modelling (I Do)	Group Work (We Do)	Independent Work (You Do)	Notes for:
1. Discussion and conduct activities on electric circuits and the functioning of various components.	1. Students observe the activities.	1. Students arrange the various electric components.	1. Which device can change chemical energy into electric energy?

<p>2. Explain ordered motion of electrons in open and closed circuits and net charge.</p> <p>3. Explain the concepts of Electric current and Drift velocity.</p> <p>4. Discussion and explain the potential difference.</p> <p>5. Explain EMf and difference between Potential difference and EMF.</p> <p>6. Conduct experiments on V/I is a constant for a conductor and V/I is not constant in LED conductor.</p> <p>7. Explain V-I graphs, Limitations of Ohm's law and Types of conductors.</p> <p>8. Discussion and explain Electric shock.</p> <p>9. Explain and conduct experiments on factors affecting the resistance of a materials.</p> <p>10. Explain resistivity and resistivity of various materials.</p> <p>11. Discussion and explain series and parallel connection of resistors.</p> <p>12. Explain Kirchhoff's laws and Problems.</p> <p>13. Discussion and explain Electric power and overload.</p>	<p>2. Group discussion on Drude and Lorentz theory.</p> <p>3. Students derive drift speed of electron in a copper wire,</p> <p>4. Students explain the direction of electric current in terms of potential difference.</p> <p>5. Group discussion on differences between Potential difference and EMF.</p> <p>6. Students conduct experiments and describe the procedure.</p> <p>7. Students draw the V-I graphs of Ohmic and Non-Ohmic conductors.</p> <p>8. Students collect information on Electric Shock.</p> <p>9. Students verify the resistance of a conductor is proportional to the length of the conductor</p> <p>10. Students collect information on the resistivity of materials and their conductivity.</p> <p>11. Students collect information on applications of series and parallel connections in daily life.</p> <p>12. Students will solve problems on Kirchhoff's laws.</p> <p>13. What precautions should be taken to avoid the overloading of domestic electric circuits?- Discuss</p>	<p>2. Students give reasons, Why net charge is zero when the conductor is in open circuit.</p> <p>3. Students complete the homework.</p> <p>4. Students write the definition of Potential difference.</p> <p>5. Students give reasons, Why emf is called force?</p> <p>6. Students read the biography of G.S.Ohm</p> <p>7. Students express the limitations of Ohm's law</p> <p>8. Students complete the homework.</p> <p>9. Students derive $R = \rho l/A$</p> <p>10. Students complete the homework.</p> <p>11. Students will solve problems on series and parallel connections.</p> <p>12. Students write Kirchhoff's laws.</p> <p>13. Students will solve problems on electric power.</p>	<p>2. Why do all materials not act as conductors?</p> <p>3. Define Electric current ?</p> <p>4. What is the S.I unit of potential difference?</p> <p>5. Define Electro motive force.</p> <p>6. Do all materials obey Ohm's law? Explain</p> <p>7. What are Ohmic and Non-Ohmic materials?</p> <p>8. What causes electric shock in the human body?</p> <p>9. What are the factors on which the resistance of the conductor depends?</p> <p>10. What is specific resistance and write its units?</p> <p>11. Silver is a better conductor of electricity than copper. Why?</p> <p>12. What quantity is conserved in Kirchhoff's first law?</p> <p>13. What do you mean by overload?</p>
---	--	--	--

Check For Understanding Questions

1. Factual:

1. Why the potential difference is necessary to produce current in a circuit?
2. Are Kirchoff's laws applicable to AC or DC circuits?
3. Why doesn't a bird get a shock when it stands on a high voltage wire?

2. Open Ended/Critical Thinking:

1. What happens when one of the resistors in series breaks down?
2. Why is resistivity called a material property?
3. Why does overload cause damage to electric appliances?

3. Student Practice Questions & Activities:


1. Deduce the expression for the equivalent resistance of three resistors connected in series.
2. State Ohm's law. Suggest an experiment to verify it and explain the procedure.
3. Write the differences between potential difference and emf
4. Two bulbs have ratings 100 W, 220V and 60 W, 220V. Which one has the greatest resistance?
5. Explain overloading of household circuits.

TLM's (Digital+Print)

1. Used prepared Quiz paper.
2. Utilized digital classroom.
3. Provide video links QR codes, DIKSHA App
4. YouTube video links

Assessment:

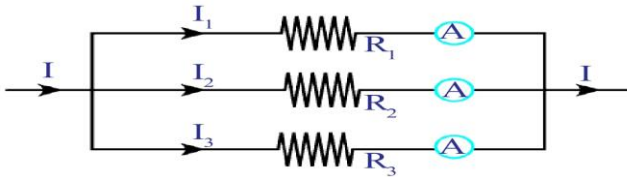1. Derive $R = \rho l/A$
2. How do you verify that resistance of a conductor is proportional to the length of the conductor for constant cross section area and temperature
3. Explain Kirchoff's laws with examples
4. Observe the figure and answer the questions.



- a) Are all the resistors connected in series or parallel?
- b) What is the equivalent resistance of the combination of three resistors?
- c) In this system, which physical quantity is constant?
- d) If $R_1 = 2 \Omega$, $R_2 = 3 \Omega$ and $R_3 = 6 \Omega$, then find equivalent resistance?

SIGNATURE OF THE TEACHER

SIGNATURE OF THE HEADMASTER

VISITING OFFICER WITH REMARKS

